

# Lecture 19 – Sequential circuits 5

Dr. Aftab M. Hussain,  
Assistant Professor, PATRIOT Lab, CVEST

## Chapter 5

# Design procedure

---

- The procedure for designing synchronous sequential circuits can be summarized by a list of recommended steps:
  1. Derive a state diagram for the circuit
  2. Assign binary values to the states
  3. Obtain the binary-coded state table
  4. Derive the simplified flip-flop input equations and output equations
  5. Draw the logic diagram

# The sequence of three detector

# Sequence of three

- Suppose we wish to design a circuit that detects a sequence of three or more consecutive 1's in a string of bits coming through an input line (i.e., the input is a *serial bit stream*)
- We start with state  $S_0$ , the reset state
- If the input is 0, the circuit stays in  $S_0$ , but if the input is 1, it goes to state  $S_1$  to indicate that a 1 was detected
- If the next input is 1, the change is to state  $S_2$  to indicate the arrival of two consecutive 1's, but if the input is 0, the state goes back to  $S_0$


# Sequence of three

---

- The third consecutive 1 sends the circuit to state  $S_3$
- If more 1's are detected, the circuit stays in  $S_3$
- Thus, the circuit stays in  $S_3$  as long as there are three or more consecutive 1's received
- The output is 1 when the circuit is in state  $S_3$  and is 0 otherwise
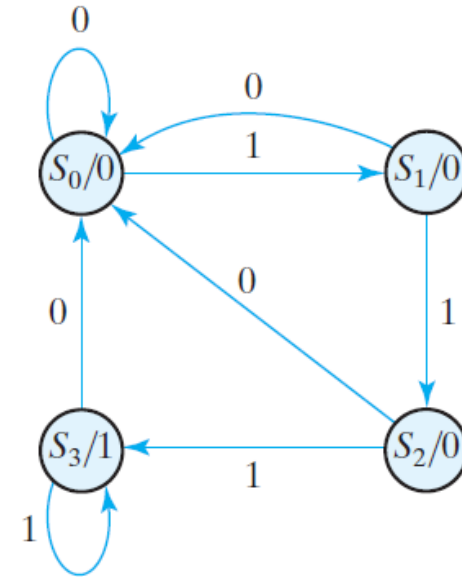
# Sequence of three

- To design the circuit, we need to assign binary codes to the states and list the state table
- The table is derived from the state diagram with a sequential binary assignment
- We choose two  $D$  flip-flops to represent the four states, and we label their outputs  $A$  and  $B$
- There is one input  $x$  and one output  $y$



Present State		Input $x$	Next State		Output $y$
$A$	$B$		$A$	$B$	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	1	1	1	1

# Sequence of three

- The flip-flop input equations can be obtained directly from the next-state columns of  $A$  and  $B$  and expressed in sum-of-minterms form as:

$$A(t + 1) = D_A(A, B, x) = \sum (3, 5, 7)$$

$$B(t + 1) = D_B(A, B, x) = \sum (1, 5, 7)$$


$$y(A, B, x) = \sum (6, 7)$$

- Using K-maps, we can find the expressions for  $D_A$ ,  $D_B$  and  $y$  as:

$$D_A = Ax + Bx$$

$$D_B = Ax + B'x$$

$$y = AB$$

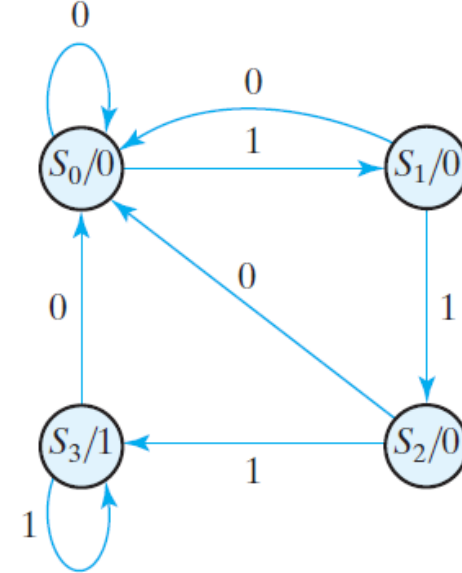

- The flip-flop input equations can be obtained directly from the next-state columns of  $A$  and  $B$  and expressed in sum-of-minterms form as:

$$A(t + 1) = D_A(A, B, x) = \sum (3, 5, 7)$$

$$B(t + 1) = D_B(A, B, x) = \sum (1, 5, 7)$$

$$y(A, B, x) = \sum (6, 7)$$


- Using K-maps, we can find the expressions for  $D_A$ ,  $D_B$  and  $y$  as:

$$D_A = Ax + Bx$$

$$D_B = Ax + B'x$$

$$y = AB$$

# Sequence of three

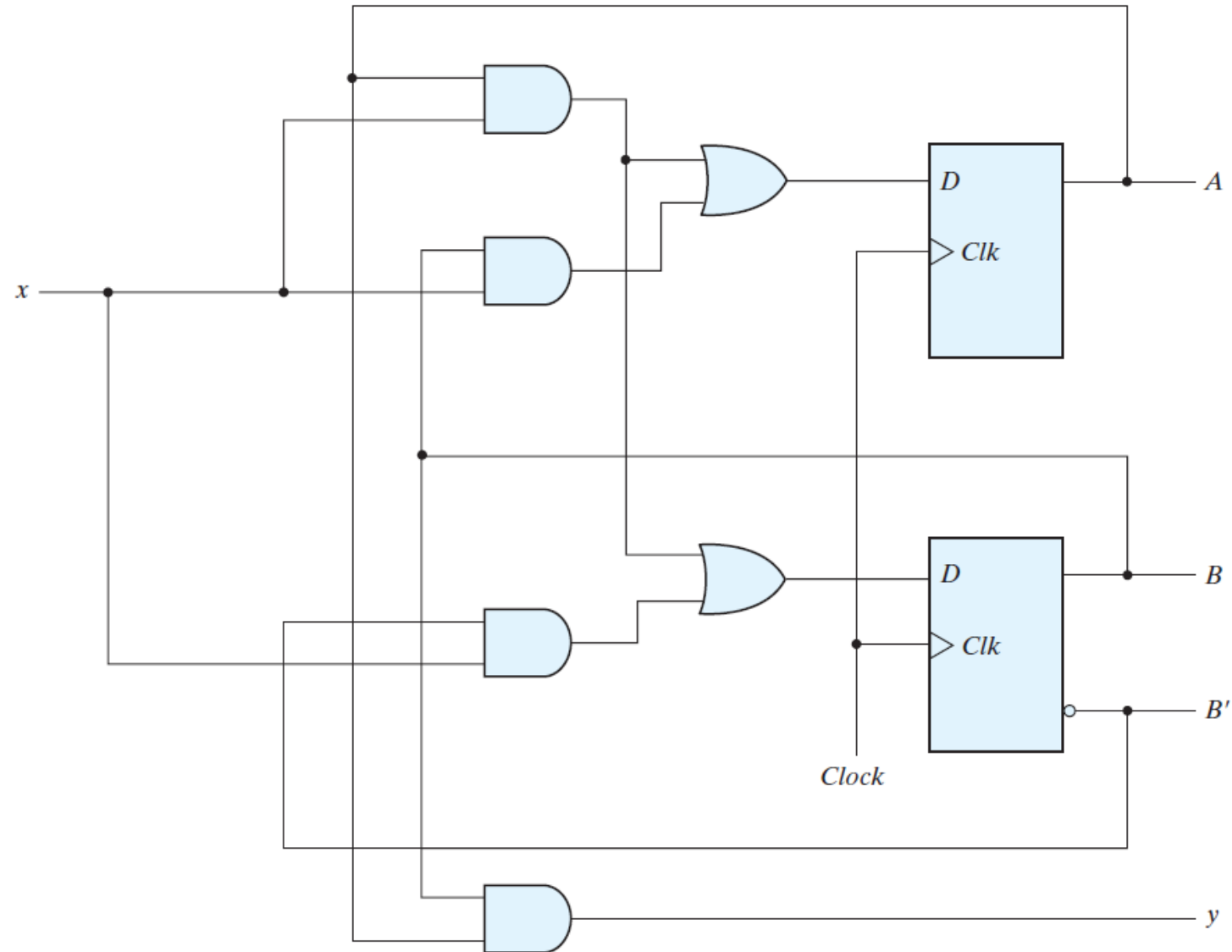




# The vending machine

# The vending machine


- Lets say we are asked to design a circuit for a vending machine that dispenses candy for Rs. 3
- The input consists of a coin slot that can accept Rs. 1 and Rs. 2 coins
- The deposit of these coins by the user is detected by a circuit that gives out two outputs x and y – when Rs. 1 is inserted, y goes to one, and when Rs. 2 is inserted, x goes to one, for one clock cycle. x and y are at zero by default
- Only one coin can be entered at once
- We need to design a circuit that takes x and y as inputs and outputs 1 if the sum is  $\geq 3$ , so that the machine can dispense the candy
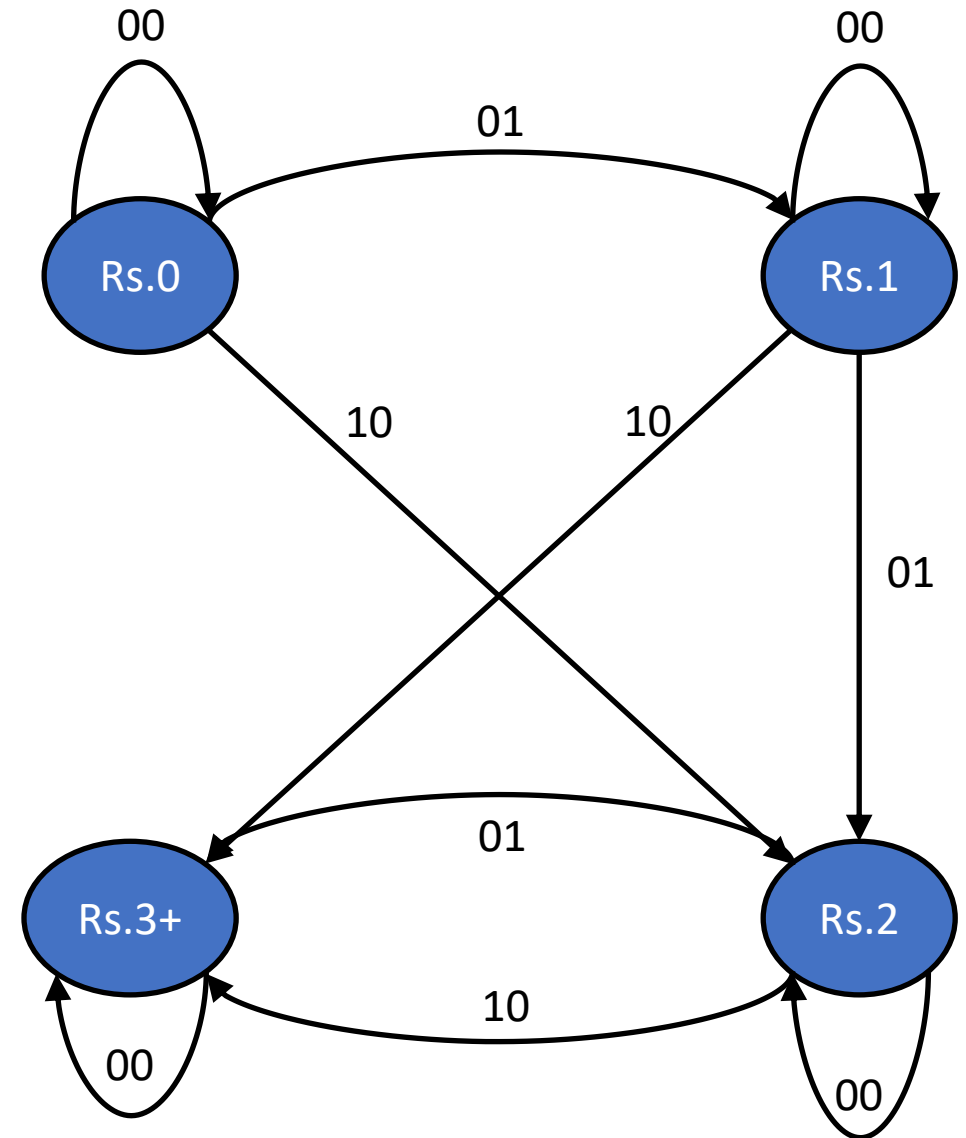
# The vending machine

- Lets say we are asked to design a circuit for a vending machine that dispenses candy for Rs. 3
- The input consists of a coin slot that can accept Rs. 1 and Rs. 2 coins
- The deposit of these coins by the user is detected by a circuit that gives out two outputs x and y – when Rs. 1 is inserted, y goes to one, and when Rs. 2 is inserted, x goes to one, for one clock cycle. x and y are at zero by default
- Only one coin can be entered at once
- We need to design a circuit that takes x and y as inputs and outputs 1 if the sum is  $\geq 3$ , so that the machine can dispense the candy




# The vending machine

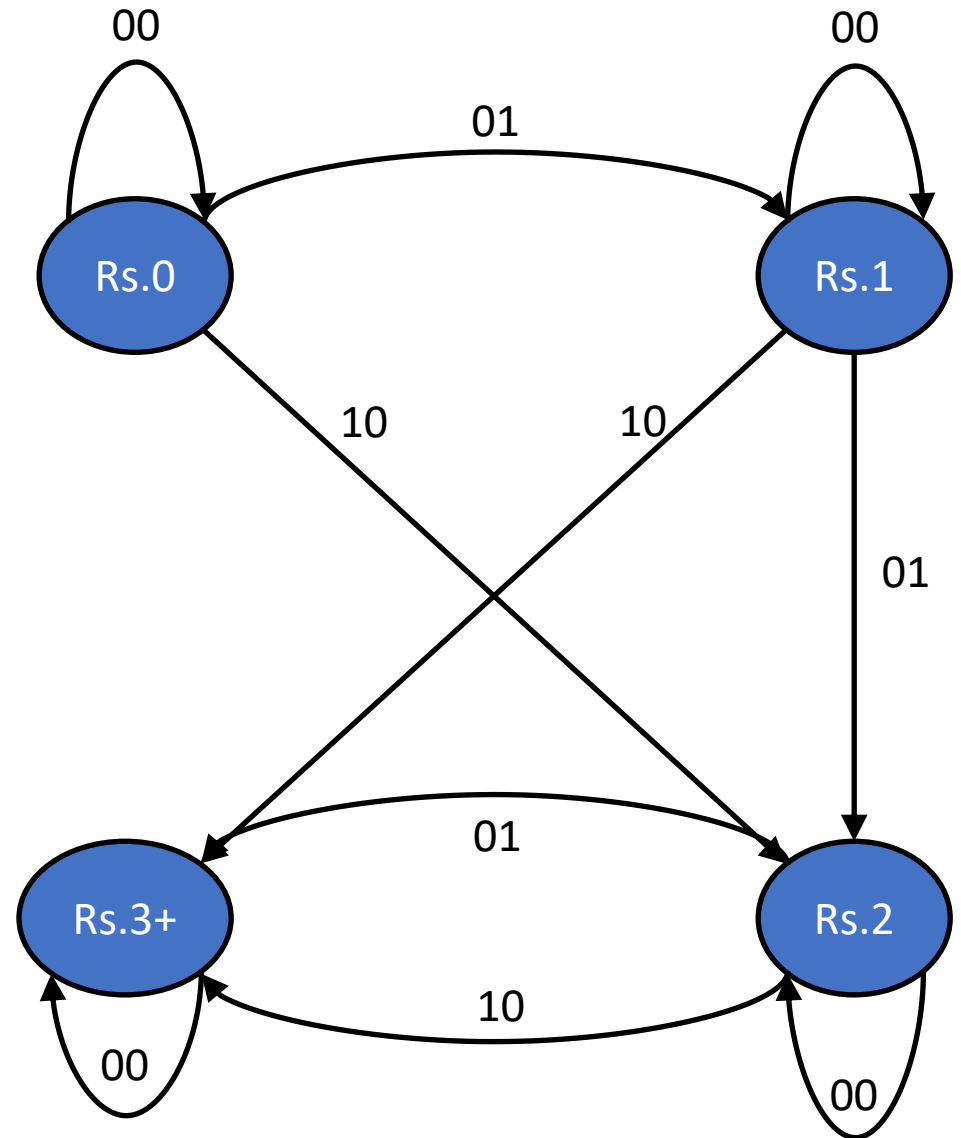

# The vending machine

A	B	x	y	A(t+1)	B(t+1)	z
0	0	0	0	0	0	0
0	0	0	1	0	1	0
0	0	1	0	1	0	0
0	0	1	1	x	x	0
0	1	0	0	0	1	0
0	1	0	1	1	0	0
0	1	1	0	1	1	0
0	1	1	1	X	X	0
1	0	0	0	1	0	0
1	0	0	1	1	1	0
1	0	1	0	1	1	0
1	0	1	1	X	x	0
1	1	0	0	1	1	1
1	1	0	1	1	1	1
1	1	1	0	1	1	1
1	1	1	1	x	x	1

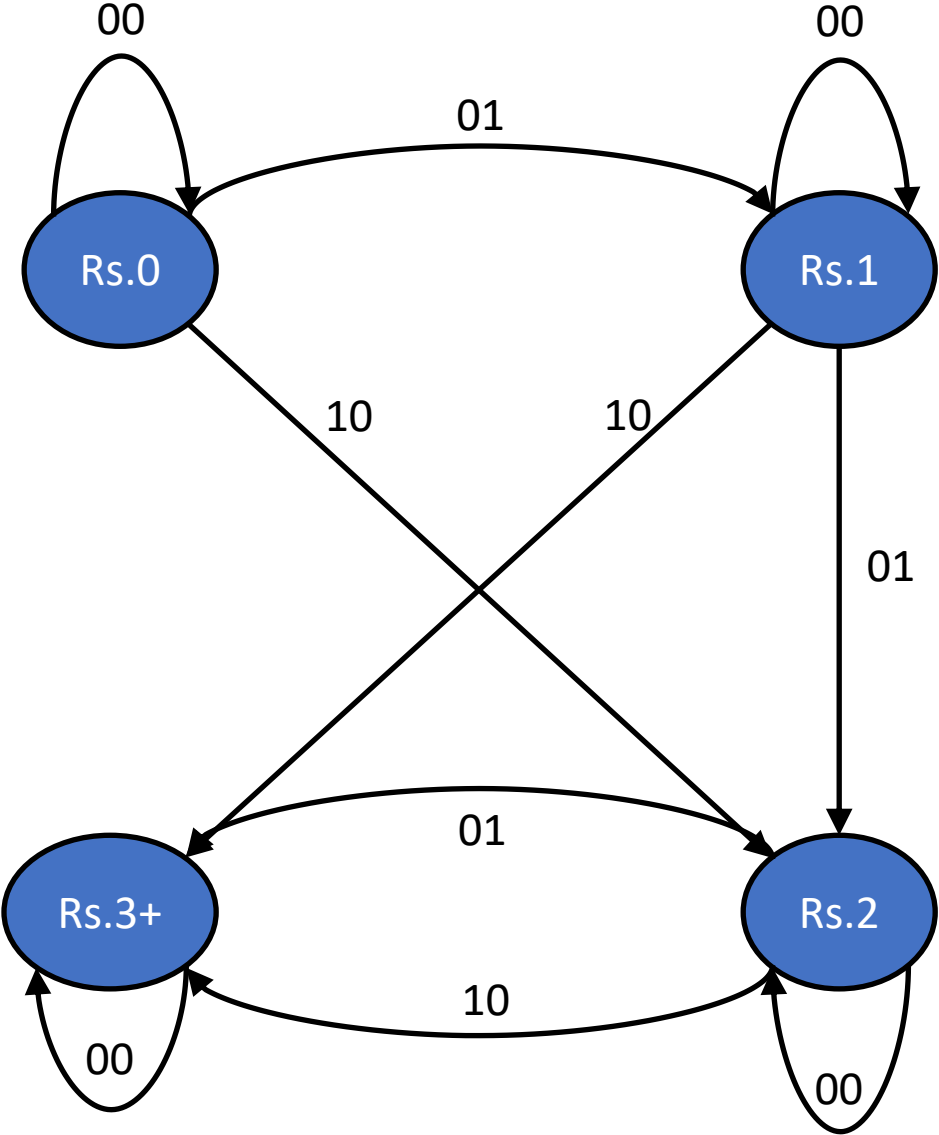

# The vending machine

$A(t+1)$

xy		x			
		00	01	11	10
AB	00	$m_0$ 0	$m_1$ 0	$m_3$ X	$m_2$ 1
	01	$m_4$ 0	$m_5$ 1	$m_7$ X	$m_6$ 1
	11	$m_{12}$ 1	$m_{13}$ 1	$m_{15}$ X	$m_{14}$ 1
	10	$m_8$ 1	$m_9$ 1	$m_{11}$ X	$m_{10}$ 1

$A$  (rows 11, 10)  
 $B$  (rows 01, 11)  
 $y$  (columns 01, 11)  
 $x$  (columns 11, 10)

$$A(t + 1) = A + x + By$$

# The vending machine

$B(t+1)$

$\begin{matrix} \text{AB} \backslash xy \\ xy \end{matrix}$		$x$			
		00	01	11	10
$A$	00	$m_0$ 0	$m_1$ 1	$m_3$ X	$m_2$ 0
	01	$m_4$ 1	$m_5$ 0	$m_7$ X	$m_6$ 1
	11	$m_{12}$ 1	$m_{13}$ 1	$m_{15}$ X	$m_{14}$ 1
	10	$m_8$ 0	$m_9$ 1	$m_{11}$ X	$m_{10}$ 1

$y$

$$B(t + 1) = (B + y + Ax)(B' + y' + A)$$