

Lecture 15 – Sequential circuits

Dr. Aftab M. Hussain,
Assistant Professor, PATRIOT Lab, CVEST

Chapter 5



The Binary Multiplier


Binary multiplier

- Multiplication of binary numbers is performed in the same way as multiplication of decimal numbers
- The multiplicand is multiplied by each bit of the multiplier, starting from the least significant bit
- Each such multiplication forms a partial product
- Successive partial products are shifted one position to the left
- The final product is obtained from the sum of the partial products
- Consider a 2-bit x 2-bit multiplier.
Number of inputs/outputs?

$$\begin{array}{r} B_1 \\ A_1 \\ \hline A_0 B_1 \\ A_1 B_0 \\ \hline C_3 C_2 C_0 \end{array}$$

Binary multiplier

- The multiplicand bits are B_1 and B_0 , the multiplier bits are A_1 and A_0 , and the product is $C_3C_2C_1C_0$
- The first partial product is formed by multiplying B_1B_0 by A_0
- The multiplication of two bits such as A_0 and B_0 produces a 1 if both bits are 1; otherwise, it produces a 0
- This is identical to an AND operation
- Therefore, the partial products can be implemented with simple AND gates
- The two partial products are added with two half-adder (HA) circuits

 


Binary multiplier

- A combinational circuit binary multiplier with more bits can be constructed in a similar fashion
- A bit of the multiplier is ANDed with each bit of the multiplicand in as many levels as there are bits in the multiplier
- The binary output in each level of AND gates is added with the partial product of the previous level to form a new partial product
- The last level produces the product
- For J multiplier bits and K multiplicand bits, we need $J * K$ AND gates and $(J - 1) K$ -bit adders to produce a product of $(J + K)$ bits
- Consider a multiplier circuit that multiplies a binary number represented by four bits by a number represented by three bits
- Let the multiplicand be represented by $B_3B_2B_1B_0$ and the multiplier by $A_2A_1A_0$

Binary multiplier

- A combinational circuit binary multiplier with more bits can be constructed in a similar fashion
- A bit of the multiplier is ANDed with each bit of the multiplicand in as many levels as there are bits in the multiplier
- The binary output in each level of AND gates is added with the partial product of the previous level to form a new partial product
- The last level produces the product
- For J multiplier bits and K multiplicand bits, we need $J * K$ AND gates and $(J - 1) K$ -bit adders to produce a product of $(J + K)$ bits
- Consider a multiplier circuit that multiplies a binary number represented by four bits by a number represented by three bits
- Let the multiplicand be represented by $B_3B_2B_1B_0$ and the multiplier by $A_2A_1A_0$

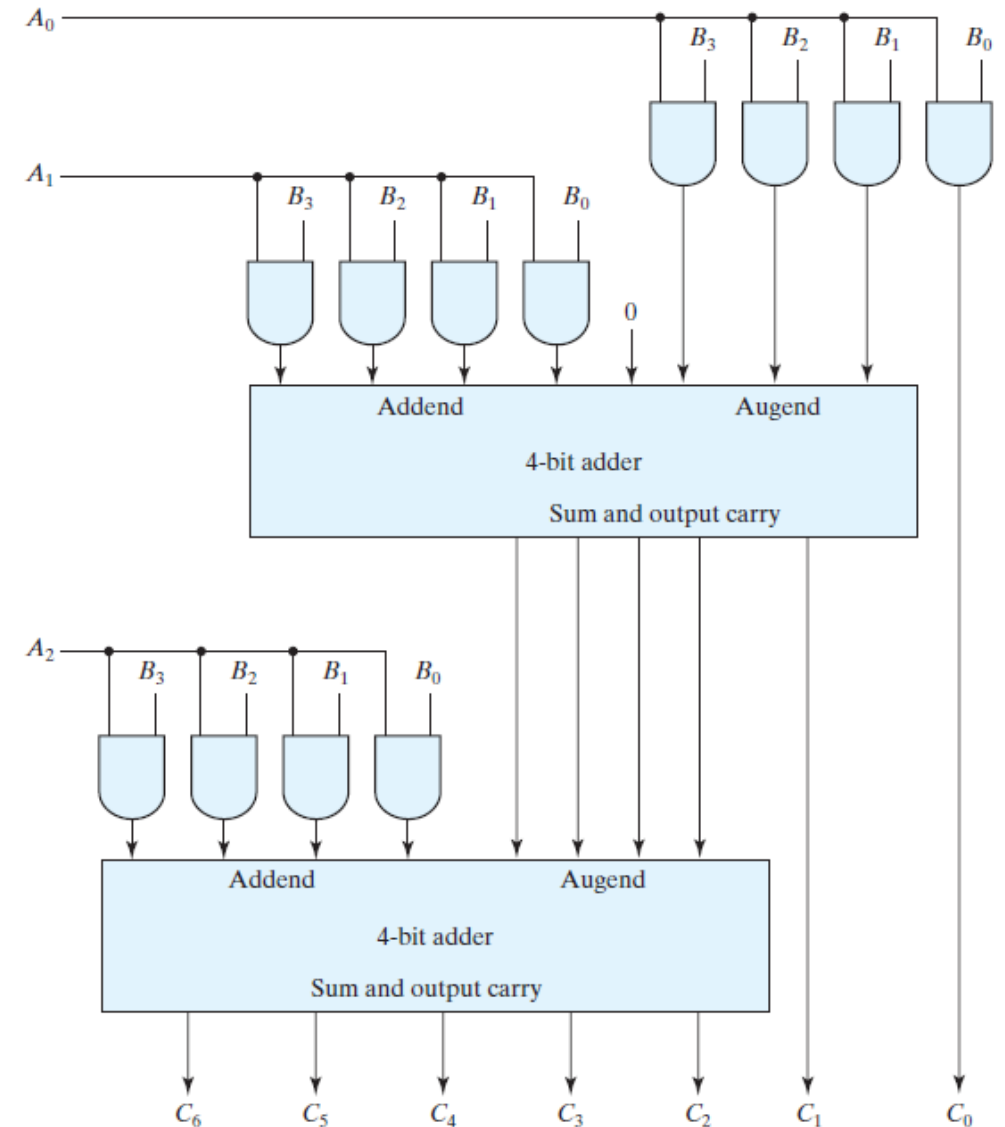



The Binary Comparator

Binary comparator

- The comparison of two numbers is an operation that determines whether one number is greater than, less than, or equal to the other number
- A *magnitude comparator* is a combinational circuit that compares two numbers A and B and determines their relative magnitudes
- The outcome of the comparison is specified by three binary variables that indicate whether $A > B$, $A = B$, or $A < B$
- On the one hand, the circuit for comparing two n -bit numbers has 2^{2n} entries in the truth table and becomes too cumbersome, even with $n = 3$
- On the other hand, as one may suspect, a comparator circuit possesses a certain amount of regularity

Binary comparator

- Consider two numbers, A and B , with four digits each $A_3A_2A_1A_0$ and $B_3B_2B_1B_0$
- The two numbers are equal if all pairs of significant digits are equal: $A_3 = B_3$, $A_2 = B_2$, $A_1 = B_1$, **and** $A_0 = B_0$
- To check bit-wise equality, we can use the XNOR gate

$$x_i = A_iB_i + A'_iB'_i \text{ for } i = 0, 1, 2, 3$$

- For equality to exist, all x_i variables must be equal to 1, a condition that dictates an AND operation of all variables:

$$(A = B) = x_3x_2x_1x_0$$

Binary comparator

- To determine whether A is greater or less than B , we inspect the relative magnitudes of pairs of significant digits, starting from the most significant position
- If the two digits of a pair are equal, we compare the next lower significant pair of digits
- The comparison continues until a pair of unequal digits is reached
- If the corresponding digit of A is 1 and that of B is 0, we conclude that $A > B$. If the corresponding digit of A is 0 and that of B is 1, we have $A < B$
- The comparison can be expressed logically by the two Boolean functions:
$$(A > B) = A_3B'_3 + x_3A_2B'_2 + x_3x_2A_1B'_1 + x_3x_2x_1A_0B'_0$$
$$(A < B) = A'_3B_3 + x_3A'_2B_2 + x_3x_2A'_1B_1 + x_3x_2x_1A'_0B_0$$

Binary comparator

$$x_i = A_i B_i + A'_i B'_i \text{ for } i = 0, 1, 2, 3$$

$$(A = B) = x_3 x_2 x_1 x_0$$


$$(A > B)$$

$$= A_3 B'_3 + x_3 A_2 B'_2 + x_3 x_2 A_1 B'_1 + x_3 x_2 x_1 A_0 B'_0$$

$$(A < B)$$

$$= A'_3 B_3 + x_3 A'_2 B_2 + x_3 x_2 A'_1 B_1 + x_3 x_2 x_1 A'_0 B_0$$

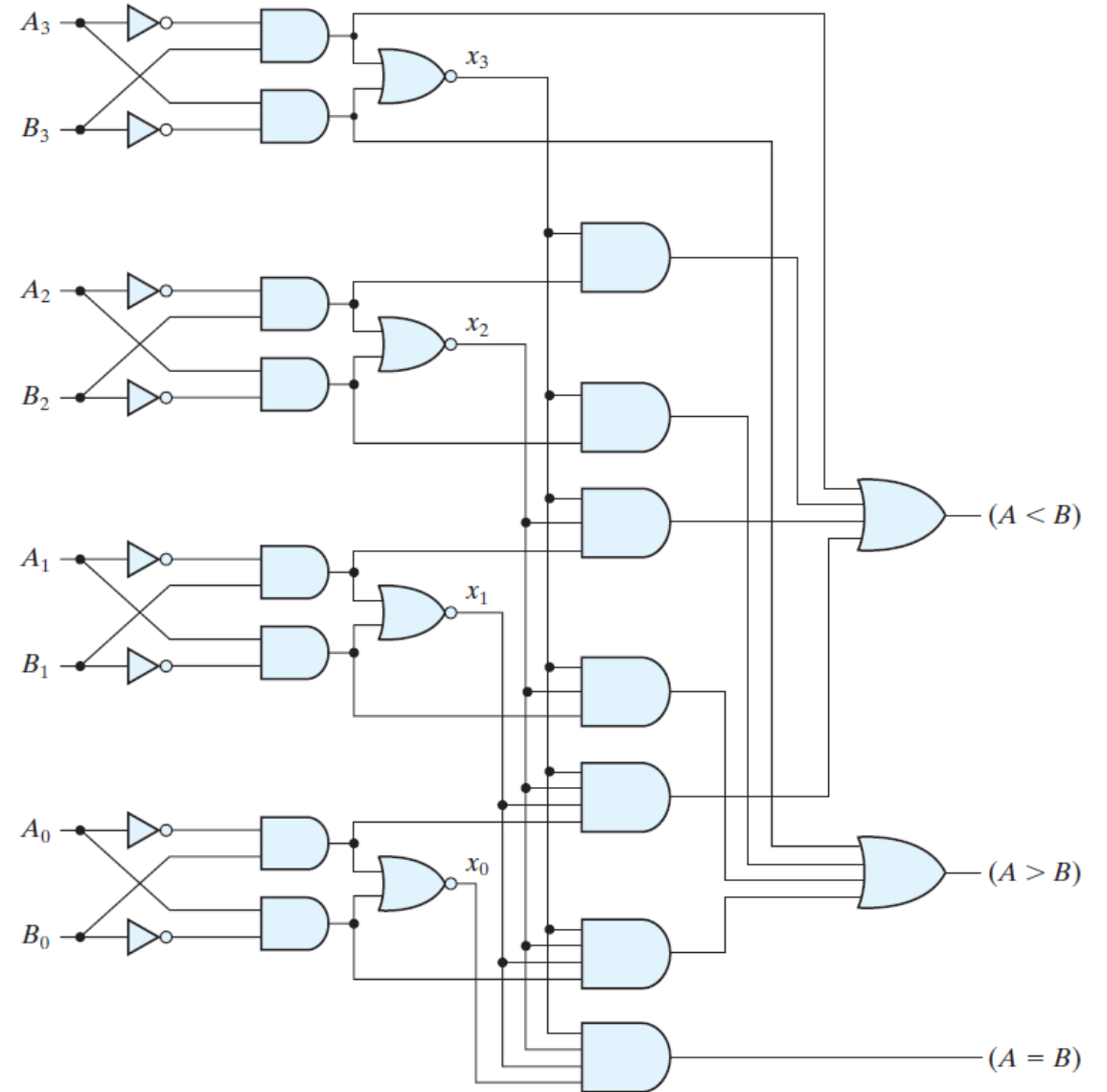Interesting: Can we prove that only one of (A=B), (A>B) and (A<B) will be “1” at any given time?





Sequential circuits

Dr. Aftab M. Hussain,
Assistant Professor, PATRIOT Lab, CVEST

Chapter 5



Gate delays

- When we apply an input to a gate, the output does not change immediately – there is a delay between the input application and appearance of the correct output
- This delay is generally of the order of nanoseconds, but can add up as signal goes through multiple gates
- *While making a digital IC design, gate delay (and by extension timing) is the single biggest consideration of all time!*
- Other things to worry about are silicon real estate, power consumption, reliability, testability, etc.

  

Glitches

- Improperly handled timing can lead to glitches and cause unexpected results
- This is particularly true for multi-level logic implementation wherein different literals are bypassing some levels
- Consider an AND gate connected to X and X'
- Such a connection will ALWAYS produce a glitch for X (0- \rightarrow 1)
- You can be sad about this glitch...
- Or you can call this circuit a “pulse generator”! 😊

  

Ring oscillators

- Another clever use of gate delays in is in the construction of ring oscillators
- It is a series of odd number of NOT gates with the output connected back to the input gate of the first gate
- With this system, we can generate a continuous square wave at Q
- What is the frequency of the wave?
- In this case, it is $f = \frac{1}{T} = \frac{1}{3 \times 2t_d}$

